
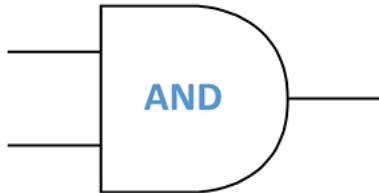


Logic gates:


AND (^)

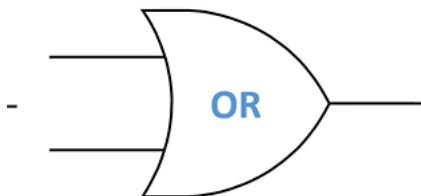

OR (V)



NOT (\neg)

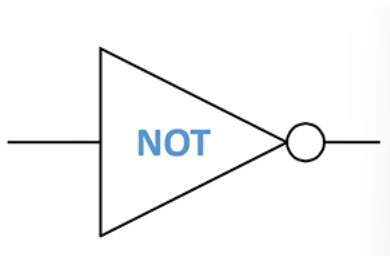

Truth tables:

Purpose of truth tables:

- Show all possible inputs
- And associated outputs

Finding all possible combinations – 2^n (inputs)

Half the number of combinations and add half of each
(0, 1)